

COMP2270 Lab 3

Due September 30 at beginning of lab

Write out solutions in a text file called 'lab3.txt' and a Logisim file called 'lab3.circ'.
Submit the homework by adding the files to your git repository.

In Git Bash, create the text file with:

```
cd ~/COMP2270-2015  
touch lab3.txt
```

Rule	Form	Dual form
Identity	$a * 1 = a$	$a + 0 = a$
Commutative	$a * b = b * a$	$a + b = b + a$
Associative	$(a * b) * c = a * (b * c)$	$(a + b) + c = a + (b + c)$
Identity	$a * 0 = 0$	$a + 1 = 1$
Distributive	$a * (b + c) = a * b + a * c$	$a + (b * c) = (a + b) * (a + c)$
Idempotence	$a * a = a$	$a + a = a$
Absorption	$a + a * b = a$	$a * (a + b) = a$
Complement	$a * a' = 0$	$a + a' = 1$
DeMorgan's	$(a + b)' = a' * b'$	$(a * b)' = a' + b'$

Use the rules above to simplify expressions. Label the rules that you apply as you apply them (no more than one rule per line).

1. Show $(a * b)' * (a' + b) * (b' + b) = a'$
2. Show $c + (b * c)' = 1$
3. Show $(a + c) * (a * d + a * d') + a * c + c = a + c$
4. Simplify $a' * (a + b) + (b + a * a) * (a + b')$
5. Show $(a' * b') + (a' * b) + (a * b') = (a * b)'$


Complete the following exercises using Logisim. Save lab3.circ in your local git repository folder.

6. Implement the majority (of 3 input bits) circuit using a 8-1 multiplexer.

X	Y	Z	Majority of X Y Z true
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

7. Implement a full adder ($a + b + \text{cin}$) using two 8-1 multiplexers (one multiplexer for carry out, one multiplexer for sum, using the same input variables).

Carry-in	A	B	Sum (A+B)	Carry-out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

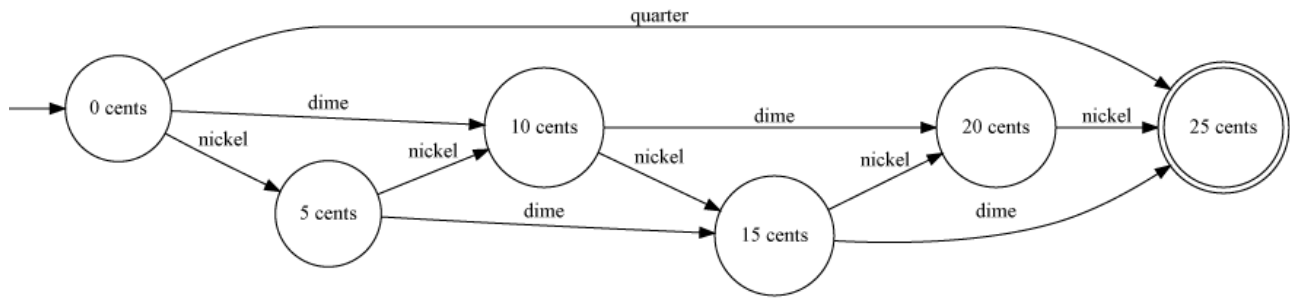

Answer the last three questions about the above finite state machine.

8.

- a. How many bits do you need to represent the states?
- b. How many bits do you need to represent the input?

9. Write a mapping from states to bits and inputs to bits.

10. Write out a state transition table that represents the machine. What happens if we dispense more than 25¢? Add a state and transitions that represent this.

In Git Bash, submit your files with:

```

cd ~/COMP2270-2015
git add lab3.txt lab3.circ
git commit -m "added lab3 files"
git push
  
```